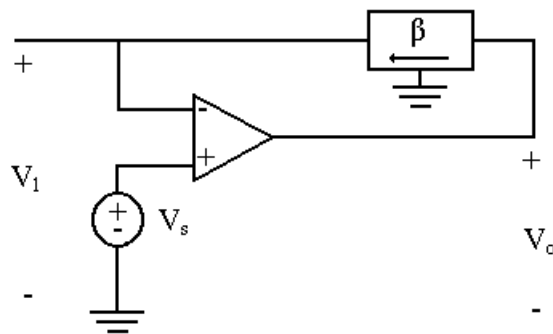


## 2.55



(α)

Αν  $A = \infty$ :

Είναι  $V_1 = V_s$  και  $V_1 = \beta V_o$  άρα:

$$\beta V_o = V_s \Leftrightarrow \frac{V_o}{V_s} = \frac{1}{\beta} \quad (1)$$

(β)

Αν  $A$  πεπερασμένο:

Είναι  $V_1 = V_s - V_o/A$  και  $V_1 = \beta V_o$  άρα:

$$\beta V_o = V_s - \frac{V_o}{A} \Rightarrow \left( \beta + \frac{1}{A} \right) V_o = V_s \Rightarrow \frac{V_o}{V_s} = \frac{1}{\beta + \frac{1}{A}} = \frac{A}{1 + A\beta} \quad (2)$$

(γ)

Αν  $A \cong \omega_t/s$ :

Είναι:

$$\frac{V_o}{V_s} = \frac{1}{\beta + \frac{s}{\omega_t}} = \frac{1/\beta}{1 + \frac{s}{\beta\omega_t}} \quad (3)$$

Άρα προκύπτει ότι  $\omega_{3dB} = \beta\omega_t$ .