

4.63

(α)

Και για τα δύο τρανζίστορες ισχύει:

$$V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2} = 15 \cdot \frac{47}{100 + 47} = 4.8 \text{ V} \quad (1)$$


$$R_B = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{100 \cdot 47}{100 + 47} = 32 \text{ k}\Omega \quad (2)$$

$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E \Rightarrow I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}} = \frac{4.8 - 0.7}{3.9 + \frac{32}{101}} = 0.97 \text{ mA} \quad (3)$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = 0.96 \text{ mA} \quad (4)$$

$$V_C = V_{CC} - I_C R_C = 8.5 \text{ V} \quad (5)$$

(β)

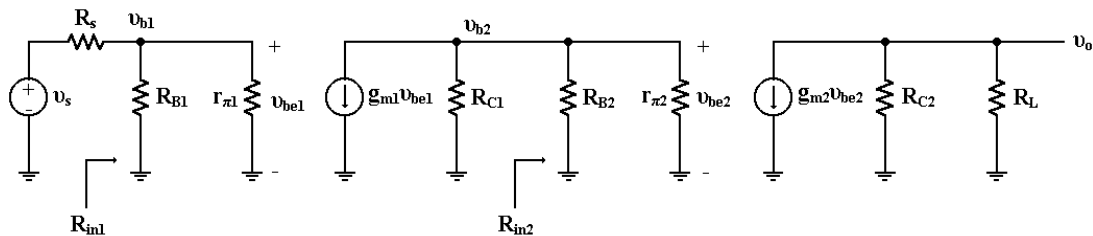

Ισχύει ότι $R_{B1} = R_{B2} = R_B = 32 \text{ k}\Omega$ και $R_{C1} = R_{C2} = R_C = 6.8 \text{ k}\Omega$. Άρα έχουμε:

$$g_{m1} = g_{m2} = \frac{I_C}{V_T} = \frac{0.96}{0.025} = 38.4 \text{ mA/V} \quad (6)$$

$$r_{\pi1} = r_{\pi2} = \frac{\beta}{g_m} = \frac{100}{38.4} = 2.6 \text{ k}\Omega \quad (7)$$

$$r_{o1} = r_{o2} = \infty \quad (8)$$

(γ)

$$R_{in1} = R_{B1} // r_{\pi1} = 2.4 \text{ k}\Omega \quad (9)$$

$$\frac{v_{b_1}}{v_s} = \frac{R_{in_1}}{R_s + R_{in_1}} = \frac{2.4}{5 + 2.4} = 0.32 V/V \quad (10)$$

(δ)

$$R_{m_2} = R_{B_2} // r_{\pi_2} = 2.4 k\Omega \quad (11)$$

$$\frac{v_{b_2}}{v_{b_1}} = -g_{m_1} (R_{C_1} // R_{m_2}) = -38.4 \cdot \frac{6.8 \cdot 2.4}{6.8 + 2.4} = -68.1 V/V \quad (12)$$

(ε)

$$\frac{v_o}{v_{b_2}} = -g_{m_2} (R_{C_2} // R_L) = -38.4 \cdot \frac{6.8 \cdot 2}{6.8 + 2} = -59.3 V/V \quad (13)$$

(στ)

Το συνολικό κέρδος τάσης είναι:

$$\frac{v_o}{v_s} = \frac{v_{b_1}}{v_s} \cdot \frac{v_{b_2}}{v_{b_1}} \cdot \frac{v_o}{v_{b_2}} = 0.32 \cdot (-68.1) \cdot (-59.3) = 1292.2 V/V \quad (14)$$